

2021
B.A./B.Sc.
Third Semester
 CORE – 7
PHYSICS
Course Code: PHC 3.31
 (Digital Systems & Applications)

PART-B
 Total Mark: 30

Answer the following questions.

1. (a) Explain the transistor as a switch. Design an OR gate by using the transistors as a switch. 2
 (b) Show that NOR gate is a universal building block. 2
 (c) Construct a 3 input EX-OR gate and show it as an odd and even parity checker. 2

 2. (a) Reduce the following Boolean expression using the K-Map:

$$F(A,B,C,D) = \sum(1, 3, 4, 5, 6, 7, 12, 13)$$
 3
 (b) Explain a circuit diagram of a 4-bit binary adder. Verify the circuit for the following operation:

$$1110 + 1001 \qquad \qquad \qquad 2+1=3$$

 3. (a) Define the term "race around condition". Explain how this condition is avoided with the help of master-slave J-K flip flop. For a given clock, draw the output waveform for a J-K flip flop in a toggle mode. 2+1=3
 (b) With the help of a circuit diagram explain how a 3-bit data in a serial mode is transferred serially. 3

 4. (a) What is the difference between synchronous and asynchronous counter? 2
 (b) Design a 4-bit asynchronous (ripple) counter. Show the output waveform of each stage. Construct a truth table for counting the clock pulse. 4

 5. (a) What are the various registers in 8085? Explain the function of Program Counter and Stack Pointer. 2
 (b) Explain 1-byte, 2-byte and 3-byte instruction for 8085 μ P, with one example each. 2
 (c) What are the different modes of data addressing? Give example of each mode. 2
-