

**2022**  
**B.A./B.Sc.**  
**Fourth Semester**  
 CORE – 10  
**PHYSICS**  
*Course Code: PHC 4.31*  
 (Analog Systems & Applications)

Total Mark: 70


Pass Mark: 28

Time: 3 hours

Answer five questions, taking one from each unit.

**UNIT-I**

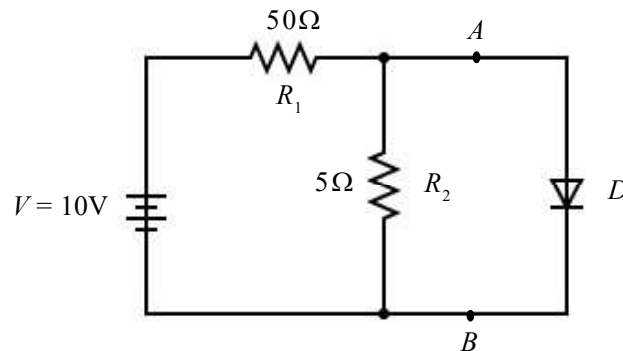1. (a) What is an intrinsic semiconductor? Show that, for pure semiconductor the conductivity is given by  $\sigma_i = en_i (\mu_n + \mu_p)$ , where symbols have their usual meanings. 5
- (b) Find the current through the diode in the circuit shown in the figure. Assume the diode to be ideal. 4



- (c) Show that for p-n junction diode, the electrostatic potential (V) across the barrier is given by  $V(x) = -\int_{x_0}^x F dx$ , where  $F$  is the barrier field. 5
2. (a) Prove that the dynamic resistance of p-n junction diode is given by  $r_{ac} = \frac{dv}{di} = \frac{\eta}{39(I + I_s)}$ , where the symbols have their usual meanings. 4

- (b) The current flowing through a silicon p-n junction diode is 60 mA for a forward bias of 0.9 volt at a temperature ( $V_{cf}$ ) 300 K.

Determine the static resistance. 3

- (c) The concentration of electrons  $n$  and holes  $p$  for an intrinsic semiconductor at a temperature  $T$  can be expressed as

$$n = p = AT^{\frac{3}{2}} \exp\left(\frac{-E_g}{2K_B T}\right); \text{ where } E_g \text{ is band gap and } A \text{ is a constant.}$$


If the mobility of both type of carrier is proportional to

$T^{-\frac{3}{2}}$ , and logarithm of the conductivity is a linear function of  $1/T$ , find the slope of the linear equation. If the slope is  $2/5$ , what is the band gap? 7

## UNIT-II

3. (a) What is the basic difference between rectifier diode and Zener diode? Explain the use of Zener diode as a voltage regulator. 5

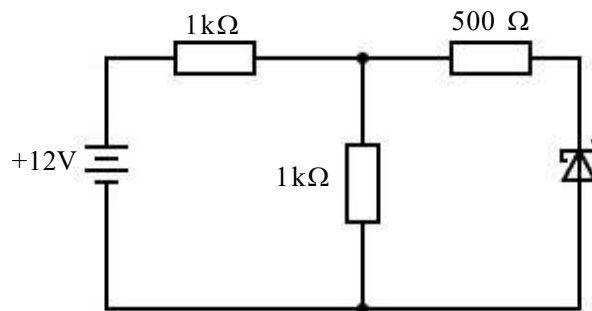- (b) In the circuit, the Zener diode has a breakdown voltage  $V_Z = 3 \text{ V}$ . Find whether the power dissipated in the Zener diode exceeds the maximum power limit of 20 mW specified for it. 4




- (c) Define ripple factor for a rectifier. Find the ripple factor of a rectifier with respect to the r.m.s. values of voltage and current. 5
4. (a) Define current amplification factors  $\alpha$  and  $\beta$ . Prove that, for a transistor,  $\beta = \frac{\alpha}{1 - \alpha}$ , where symbols have their usual meanings. 5

- (b) Consider an n-p-n transistor in common base mode with base current  $I_B = 0.05$  mA and reverse saturation current is  $10 \mu\text{A}$ . If the DC current gain is 0.98, find the emitter current and collector current. 4
- (c) Draw and explain the input and output characteristics of common emitter transistor. 5

### UNIT-III

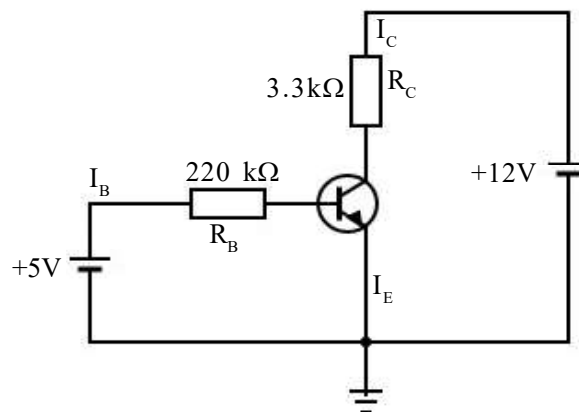
5. (a) Explain briefly load and quiescent point for a transistor amplifier. Write down the factors determining the choice of quiescent point and its stability factors. What is thermal run away? 7
- (b) Explain transistor as a two port device and find h-equivalent circuit. Determine the h-parameters from transistor characteristics. 7
6. (a) What do you mean by transconductance of a transistor? If the input impedance, forward current gain of a CB transistor are  $h_{ib}$  and  $h_{fb}$ , find the conversion formulae for the CE configuration. 7
- (b) A silicon transistor having  $\beta = 1000$  and  $I_{CO} = 22$  nA is operated in the CE configuration. Assuming  $V_{BE} = 0.7$  V, determine the transistor current and region of operation. What happens if the load resistance  $R_C$  is indefinitely increased? 7



### UNIT-IV

7. (a) What do you mean by feedback in amplifier? Mention different types of feedback networks. Find the expression for transfer gain of a voltage series feedback amplifier in CE configuration. 5

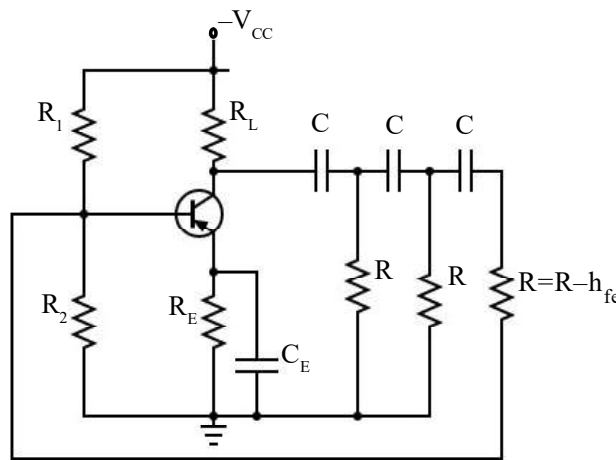
- (b) Explain briefly the effect of negative feedback on the performance of an amplifier. 3
- (c) Define transconductive and transresistive feedback fractions. Explain with mathematical expressions, how stability of gain can be increased by using negative feedback in electronic circuit? 6
8. (a) Define the Barkhausen criterion for sustained oscillations. Derive the condition for sustained oscillation and frequency of oscillation for Wien bridge oscillator. 7
- (b) Find the frequency of oscillation for sustained oscillation for the given RC oscillator circuit. 7




### UNIT-V


9. (a) Write the characteristics of ideal and practical op-amps. What is CMRR? Find its expression. 4
- (b) Explain with proper diagram and expression, the use of op-amps as a differentiator. 4
- (c) What is virtual ground for an op-amp circuit? Calculate the output voltage  $V_o$  for the following circuits. 6

(i)

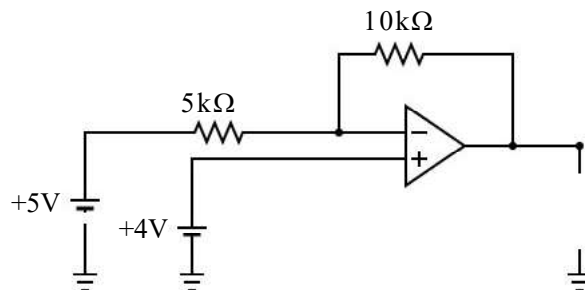

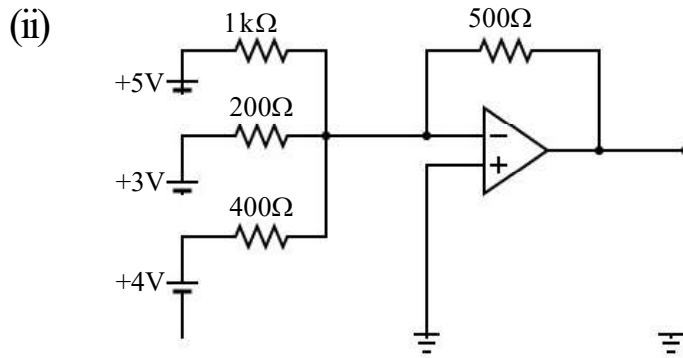

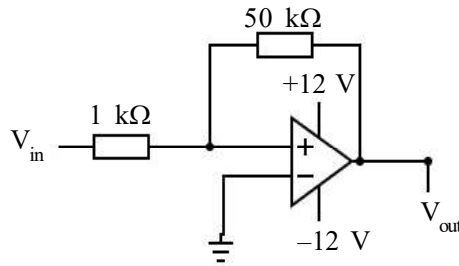10. (a) Define offset error voltage and current for an open loop op-amp. 2  
 (b) Compute the voltage gain for the op-amp as shown in the figure. Find the output voltage  $V_{out}$  if the input voltage is  $V_{in} = 0.5 \sin(100\pi t)$ . Draw the corresponding input and output signals. 7



- (c) Find the output for the different stages of op-amp. 5

