

April 2025
B.A./B.Sc.
Fourth Semester
CORE – 10
PHYSICS
Course Code: PHC 4.31
(Digital Systems & Applications)

Total Mark: 70

Pass Mark: 28

Time: 3 hours

Answer five questions, taking one from each unit.

UNIT-I

1. (a) Discuss XOR gate with necessary circuit diagram and write its truth table. 5
- (b) What is parity checker? Explain how XNOR gate is used as odd parity checker. 1+4=5
- (c) Explain the operation of OR gate using a transistor. 4
2. (a) Write a short note on emitter coupled logic circuit. 6
- (b) (i) Convert 110101 to decimal number. 1
- (ii) Convert 95.5 to hexadecimal number. 1
- (c) Illustrate how a NAND gate can be used to design a AND, OR and NOT gate. 3
- (d) What is an integrated circuit (IC)? List some of the advantages of IC. 1+2=3


UNIT-II

3. (a) A three variable truth table has a high output for these input conditions: 000, 010, 100 and 110. What is the sum of products circuit? Simplify the sum of product equations. 5
- (b) Simplify the Boolean expression $\overline{X\overline{Y}} + XYZ + X(Y + X\overline{Y})$ 4
- (c) Explain half adder with help of a circuit diagram. 5

4. (a) Draw the logic circuit for the Boolean expression:
 $Y = \bar{A}\bar{B}CD + A\bar{B}\bar{C}D + AB\bar{C}\bar{D} + \bar{A}BC\bar{D}$. Draw the corresponding Karnaugh map. 2+1=3
- (b) Prove that $A(\bar{A} + C)(\bar{A}B + C)(\bar{A}BC + C) = 0$ 5
- (c) Explain a 1:4 demultiplexer. 6

UNIT-III

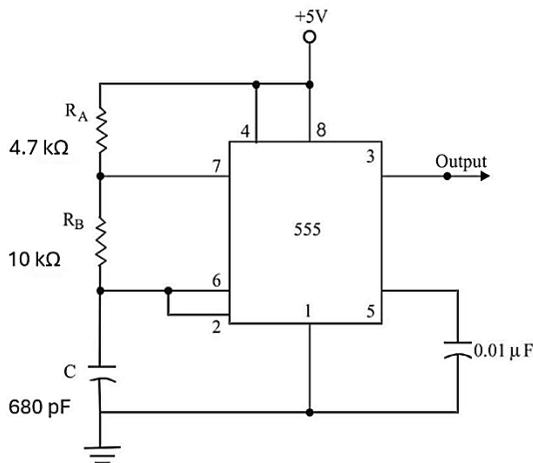5. (a) Draw logic circuit diagram of J-K flip-flop using NAND gate and explain it with necessary truth table and its timing diagram. 6
- (b) Explain the operation of preset and clear condition. 5
- (c) Differentiate between positive and negative edge triggering. 3
6. (a) Explain serial input parallel output shift register. 5
- (b) Draw logic circuit diagram of D flip-flop and explain the truth table with timing diagram. 5
- (c) An astable multivibrator circuit using 555 timer is shown in figure. Determine the time interval of charging (t_1), discharging (t_2), frequency and duty cycle of the output waveform. 4



UNIT-IV

7. (a) With the aid of a neat diagram, explain the operation of 3 bit asynchronous counter. 6
- (b) Write a short note on random access memory (RAM). 4

- (c) Discuss about cache memory with help of a block diagram. 4
- 8. (a) Explain a 4 bit decade counter. 6
- (b) Describe memory interfacing and its requirements for minimum mode memory interfacing. 4
- (c) Elaborate on the input/output devices of computer organisation. 4

UNIT-V

- 9. (a) With the help of a neat diagram, explain the architecture of 8085 microprocessor. List the features of 8085 microprocessor. 5+3=8
- (b) Discuss the description of timing and control unit in 8085 microprocessors. 6
- 10. (a) Explain different types of addressing modes in 8085, with example. 5
- (b) Draw the timing diagram of MVI A, data instruction and explain its operation. 4
- (c) Describe the function of special purpose registers in 8085 microprocessor. 5
