

2023
B.A./B.Sc.
Fourth Semester
CORE – 10
PHYSICS
Course Code: PHC 4.31(R)
(Analog Systems & Applications)

Total Mark: 70
Time: 3 hours

Pass Mark: 28

Answer five questions, taking one from each unit.

UNIT-I

1. (a) What is an energy level diagram? Explain the energy-level diagram for hydrogen. 1+3=4
(b) Explain why a semiconductor acts as an insulator at 0°K and why it's a conductivity increases with increasing temperature. 3
(c) Define drift velocity. With the help of a proper circuit diagram derive an expression for electron drift velocity. 2+5=7

2. (a) The seven lowest energy levels of sodium vapour are 0, 2.10, 3.19, 3.60, 3.75, 4.10 and 4.26 eV respectively. A photon of wavelength 3300 \AA is absorbed by an atom of the vapour.
 - (i) What are all the possible florescent lines that may appear?
 - (ii) If three photons are emitted and one of these is $11,380\text{ \AA}$ line, what are the wavelength of the other two photon? 2+2=4
(b) Explain the barrier formation in a PN junction diode. 3
(c) Explain in detail the difference in current flow mechanism in a forward and reverse-biased diodes. 7

UNIT-II

3. (a) With a circuit diagram explain the input signal rectification by a centre-tapped rectifier. What is it's rectification efficiency? 4+2=6
(b) Explain the principle and structure of a LED. 4
(c) Explain the VI characteristics of CC transistor. 4

4. (a) What is a Zener diode? Explain how it can be used as a voltage regulator. 2+4=6
- (b) Obtain the ripple factor of a bridge rectifier. 3
- (c) Plot a neat output characteristic of CB-Transistor and hence explain:
- (i) Active region
 - (ii) Cut-off region
 - (iii) Saturation region 5

UNIT-III

5. (a) Define stability factor. Calculate the stability factor for CB and CE circuits. 2+4=6
- (b) Draw the circuit diagram of a transistor with voltage divider bias. Explain the working and hence show that the DC bias circuit is independent of B. 2+4=6
- (c) Differentiate between a class A and a class B amplifier. 2
6. (a) Give a detailed analysis of a single stage CE amplifier using hybrid model. What is its output impedance? 4+2=6
- (b) With proper circuit diagram explain the operation of a two-stage RC coupled amplifier. Also explain its frequency response. 8

UNIT-IV

7. (a) What is the advantage of negative feedback over positive feedback in an amplifier. 2
- (b) In a negative-feedback amplifier, $A = 100$, $B = 0.04$ and $V_i = 50$ mV. Find
- (i) gain with feedback
 - (ii) output voltage
 - (iii) feedback factor
 - (iv) feedback voltage 4
- (c) Explain the principle and working of a RC phase-shift oscillator. Obtain an expression for the oscillation frequency. 8
8. (a) Explain in brief the effect of negative feedback on the gain and bandwidth of the amplifier. 4

- (b) With a proper circuit diagram explain a Hartley oscillator and its oscillator. Also, find its operation frequency. 8
- (c) A Colpitt's oscillator having $L = 100 \mu\text{H}$, $L_{RFC} = 0.5 \text{ mH}$, $C_1 = 0.005 \mu\text{F}$, $C_2 = 0.01 \mu\text{F}$, and $C_C = 10 \mu\text{F}$, find the oscillation frequency. 2

UNIT-V

9. (a) For an op-amp having a slew rate of $SR = 2 \text{ V}/\mu\text{s}$, what is the maximum closed-loop voltage gain that can be used when the input signal varies by 0.5 V in $10 \mu\text{s}$. 3
- (b) Determine the output voltage of an op-amp for input voltages of $V_{i1} = 150 \mu\text{V}$ and $V_{i2} = 140 \mu\text{V}$. The amplifier has a differential gain of $A_d = 4000$ and $\text{CMRR} = 100$. 3
- (c) Explain with proper circuit diagram, the application of op-amp as
 (i) differentiator
 (ii) log amplifier 5
- (d) With proper circuit explain in brief the operation of an n-bit R-2R resistor ladder. 3
10. (a) Show the circuit and explain how to measure A_v and R_i of an op-amp. 2
- (b) Draw the schematic diagram of an ideal inverting op-amp with voltage-shunt feedback impedances Z and Z' , and indicate the virtual-ground model for calculating the gain. 4
- (c) A 5 mV , 1 kHz sinusoidal signal is applied to the input of an op-amp integrator for which $R = 100 \text{ K}$ and $C = 1 \mu\text{F}$. Find the output voltage. 3
- (d) For an ideal inverting amplifier with $R_1 = 1 \text{ K}$ and $R_f = 1 \text{ M}$, determine
 (i) voltage gain
 (ii) input resistance
 (iii) output resistance 3
- (e) Define weighted network with a circuit diagram. 2

