

2022
B.A./B.Sc.
Third Semester
 CORE – 7
PHYSICS
Course Code: PHC 3.31
 (Analog Systems & Applications)

Total Mark: 70

Pass Mark: 28

Time: 3 hours

Answer five questions, taking one from each unit.

UNIT-I

1. (a) Explain the two types of extrinsic semiconductors. 2
- (b) Explain the barrier formation in PN junction diode. 3
- (c) Pure silicon at 300 K has equal electron and hole concentration of 1.5×10^{16} per m^3 . Doping with indium increases n_h to 4.5×10^{22} per m^3 . Calculate n_e in the doped silicon. 2
- (d) Derive the expression for barrier potential of a PN junction diode. 7
2. (a) Briefly explain the resistance in a PN junction diode. 3
- (b) Explain the I-V characteristics of PN junction diode. 4
- (c) Derive the expression for space charge width of a PN junction diode. 7

UNIT-II

3. (a) What is ripple factor? Derive the expression for DC, rms, efficiency and ripple factor of a full wave rectifier. 1+5=6
- (b) Explain the working of a Zener diode and its role in voltage regulation. 4
- (c) A transistor using potential divider network biasing has the following values: $R_1 = 50 \text{ k}\Omega$, $R_2 = 10 \text{ k}\Omega$, $R_E = 1 \text{ k}\Omega$, $V_{CC} = 12 \text{ V}$ and $V_{BE} = 0.1 \text{ V}$. Find I_C . 2

(d) A full bridge rectifier uses two diodes. The forward bias resistance of each diode is $25\ \Omega$. The transformer rms secondary voltage is

$50\sqrt{2}$ volt and load resistance of $1475\ \Omega$. Find: 1+1=2

- (i) Mean load current
- (ii) RMS value of load current

4. (a) Explain the working of a full wave rectifier. Explain the role of C filter in the signal rectification. Draw circuit diagrams wherever necessary. 3+2=5

(b) What is a Zener diode? Explain how it can be used as a voltage regulator. 1+4=5


(c) Plot a neat output characteristic graph of a CE transistor and hence explain: 4

- (i) Active region
- (ii) Cut-off region
- (iii) Saturation region

UNIT-III

5. (a) Explain the working of a CE amplifier with the help of circuit diagram. Plot the output characteristics of a CE biased amplifier with input and output signals. 4+2=6

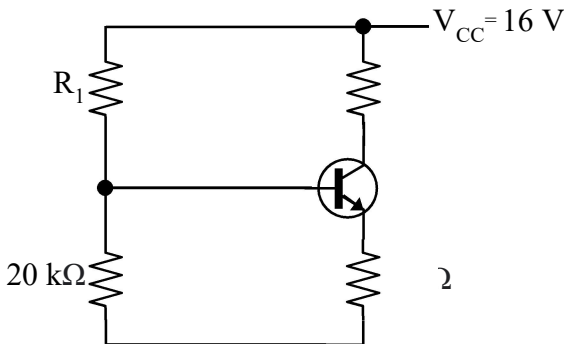(b) An n-p-n transistor circuit has $\alpha = 0.985$, $V_{BE} = 0.3\ \text{V}$. If $V_{CC} = 16\ \text{V}$, calculate R_1 and R_C to test the Q point at $I_C = 2\ \text{mA}$, $V_{CE} = 6\ \text{V}$. 4



- (c) What is the significance of Q-point? Differentiate between class A and class B power amplifiers. 1+3=4
6. (a) Using h-parameters, derive the expression for current gain (A_i), voltage gain (A_v) input impedance (Z_i) and output impedance (Z_o). 6
- (b) Explain the R-C working of coupled amplifier with the help of circuit diagram. Also, explain the frequency response curve of R-C coupled amplifier 3+3=6
- (c) What is the significance of 3 dB point in context of amplifier? 2

UNIT-IV

7. (a) Explain positive feedback and negative feedback of an amplifier. 2
- (b) Explain in detail the different advantages of a negative feedback amplifier. 8
- (c) In a negative feedback amplifier, $A = 100$, $\beta = 0.04$. Find: 4
- (i) Gain with feedback
- (ii) Output voltage
- (iii) Feedback voltage
- (iv) Loop gain
8. (a) What do you mean by feedback in amplifiers? 2
- (b) With the help of a circuit diagram describe the operation of a Colpitts oscillator. Derive the expression for the frequency produced by the Colpitts oscillator. 3+7=10
- (c) A Colpitts oscillator have $L = 100 \mu\text{H}$, $C_1 = 0.005 \mu\text{F}$, $C_2 = 10 \mu\text{F}$. Find the oscillation frequency. 2

UNIT-V

9. (a) Explain with proper circuit diagram, the application of op amp as a/an: 8
- (i) Integrator
- (ii) Adder
- (iii) Differentiator
- (iv) Log amplifier

- (b) With the help of a block diagram explain the basic elements of an operational amplifier (op amp). State the characteristics of an ideal op amp. 6
10. (a) Define common mode rejection ratio (CMRR), slew rate and virtual ground. 3
- (b) Determine the output voltage of an op amp for input voltages of $V_{i1} = 150 \mu\text{V}$, $V_{i2} = 140 \mu\text{V}$. The amplifier has a differential gain of $A_d = 4000$ and $\text{CMRR} = 100$. 3
- (c) With the help of a circuit diagram explain the function of an inverting amplifier. Derive an expression for voltage gain of an inverting amplifier. 5
- (d) For an ideal inverting amplifier with $R_1 = 1 \text{ k}\Omega$, and $R_f = 1 \text{ M}\Omega$, determine: 3
- (i) Voltage gain
 - (ii) Input resistance
 - (iii) Output resistance
-