

**2023**  
**B.A./B.Sc.**  
**Third Semester**  
 CORE – 7  
**PHYSICS**  
*Course Code: PHC 3.31*  
 (Analog Systems & Applications)

*Total Mark: 70*  
*Time: 3 hours*

*Pass Mark: 28*

*Answer five questions, taking one from each unit.*

**UNIT-I**

1. (a) Explain the working of forward biased and reverse biased PN junction using energy band diagrams. 6
- (b) Discuss the formation of  $n$  type semi-conductor and its energy band. 5
- (c) A silicon diode having a doping concentration of  $N_A = 9 \times 10^{16} \text{ cm}^{-3}$  on p-side and  $N_D = 1 \times 10^{16} \text{ cm}^{-3}$  on n-side is reverse biased with a total depletion width of  $3 \mu\text{m}$ . Given that the permittivity of silicon is  $1.04 \times 10^{-12} \text{ F cm}^{-1}$ , find the depletion width on the p-side and the maximum electric field in the depletion region. 3
2. (a) What is the difference between static and dynamic resistance of a PN junction diode? 4
- (b) A small concentration of minority is injected into a homogenous semiconductor crystal at one point. An electric field of  $10 \text{ V cm}^{-1}$  is applied across the crystal and this moves the minority carriers to a distance of  $1 \text{ cm}$  in  $20 \mu\text{sec}$ . Calculate the mobility (in  $\text{cm}^2 \text{ V}^{-1} \text{ s}^{-1}$ ). 4
- (c) Discuss I-V characteristics of a p-n junction diode and obtain an expression for its static and dynamic resistance from the diode equation. 6

## UNIT-II

3. (a) Draw the common emitter characteristic using a p-n-p transistor. Explain the input and output characteristics. 2+4=6
- (b) What is a load line? Explain how a load line is plotted. What is the significance of points of interception of a load line with the curves of output characteristics? 1+2=3
- (c) In a centre tap full wave rectifier, each diode has a forward dynamic resistance  $r = 10\Omega$  and load resistance  $R_L = 1\text{k}\Omega$ . The voltage across each half of the secondary winding is  $220 \sin 314t$ .
- Find: 5
- (i) the peak value of current
  - (ii) the dc or average value of current
  - (iii) the rms value of current
  - (iv) the ripple factor
  - (v) the rectification efficiency
4. (a) What do you mean by power dissipation and breakdown voltage range in Zener diode? 2
- (b) Draw the circuit diagram of a half wave rectifier and explain its working. Calculate the efficiency and value of ripple factor. 1+3+2+2=8
- (c) A transformer is applied with rms voltage of 230 V across a diode ( $r = 500\Omega$ ) in a circuit of half wave rectifier. If the rated output current is 80 mA, calculate the regulation and fall in its efficiency with the use of full load. 4

## UNIT-III

5. (a) Determine the current gain, input resistance and voltage gain of a Common Emitter transistor amplifier, in terms of  $h$ -parameters. 6
- (b) Show that the maximum collector efficiency in class A amplifier is 50% only. 4
- (c) The overall gain of an amplifier is 140, with negative feedback the gain gets reduced to 17.5. Find the fraction of the output that is feedback to the input? 4

6. (a) Draw the circuit diagram to explain the working of class B amplifier. 1+4=5
- (b) A transistor amplifier in CE configuration couples a source of internal resistance  $1\text{ k}\Omega$  to a load of  $20\text{ k}\Omega$ . Find the input and the output resistances if  $h_{ie} = 1\text{ k}\Omega$ ,  $h_{re} = 2.5 \times 10^{-4}$ ,  $h_{fe} = 150$  and  $\frac{1}{h_{oe}} = 40\text{ k}\Omega$ . 4
- (c) Explain how the frequency response of two staged RC coupled transistor amplifier varies with low, mid and high frequency signal. 5

#### UNIT-IV

7. (a) What is the difference between closed loop and open loop gain? 3
- (b) The frequency of a Hartley oscillator is to vary from  $60\text{ kHz}$  to  $120\text{ kHz}$ . The tuning capacitor can be changed from  $100\text{ pF}$  to  $400\text{ pF}$ . The transistor employed in the circuit has  $h_{fe} = 90$  and  $h_{re} = 0.2$ . Find the values of the inductance, neglecting the mutual inductance between them. 4
- (c) In a phase shift oscillator with  $R_1 = R_2 = R_3 = 800\text{ k}\Omega$  and  $C_1 = C_2 = C_3 = 100\text{ pF}$ , calculate the frequency of the oscillator. 2
- (d) What is Barkhausen's criterion? Explain the basic requirements for a feedback amplifier to generate the oscillations. 1+4=5
8. (a) What is the principle of phase shift oscillator? Derive an expression for the frequency of oscillations and the conditions for sustained oscillations. 1+5+2=8
- (b) Discuss the effect of input impedance for voltage-series and current-shunt feedback. 2+2=4
- (c) Find the operating frequency of transistor Colpitts's oscillator if  $C_1 = 0.001\text{ }\mu\text{F}$ ,  $C_2 = 0.01\text{ }\mu\text{F}$  and  $L = 15\text{ }\mu\text{F}$ . 2

#### UNIT-V

9. (a) Explain the operation of zero-crossing detector. 6
- (b) Discuss the op-amp when it used as an inverting and non-inverting amplifier. 3+3=6

(c) For a given operational amplifier,  $CMMR = 10^4$  and differential gain  $= 10^4$ . Determine common mode gain  $A_{CM}$  of the op-amp. 2

10. (a) Draw a neat diagram for 4-bit R-2R ladder and explain the operation of DAC. 2+4=6

(b) Calculate the output voltage of an op-amp summing amplifier for following sets of voltages and resistor. Use  $R_f = 1\text{ M}\Omega$ ,  $V_1 = 1\text{ V}$ ,  $V_2 = 2\text{ V}$ ,  $V_3 = 3\text{ V}$ ,  $R_1 = 500\text{ k}\Omega$ ,  $R_2 = 1\text{ M}\Omega$ ,  $R_3 = 1\text{ M}\Omega$ . 4

(c) Determine the full-scale output and the percentage resolution for an 8-bit DAC having step size of 5 mV. 4

